
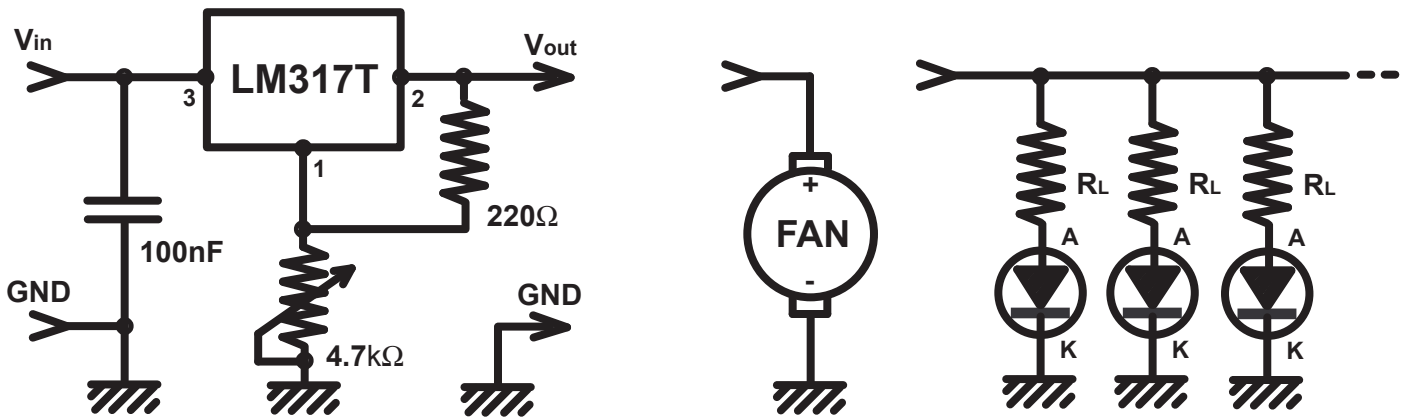


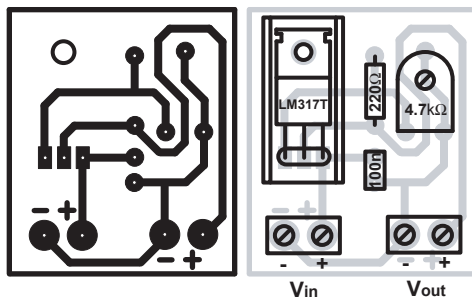
Ajustable voltage regulator using the LM 317T integrated Circuit



PCB Design



With adjustable resistor

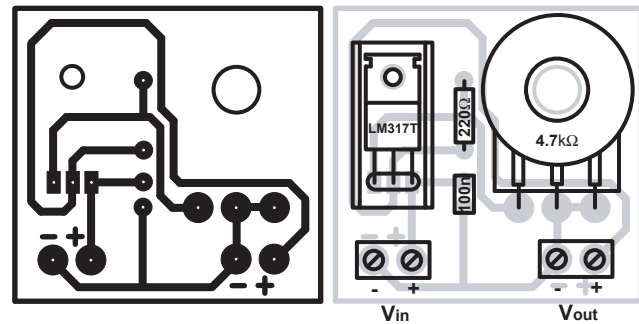

With Potentiometer

All PCB are drawn to scale and are reversed. Once printed the inked side of the paper should face the PCB.

Antoine Bercovici, 04/23/2004.